

-
- Chapter 1: Introduction
 - Chapter 2: Basic components and electric circuits
 - Chapter 3: Voltage and current laws
 - Chapter 4: Basic Nodal and Mesh analysis
 - Chapter 5: Handy circuit analysis techniques
 - Chapter 6: The Operational Amplifier
 - Chapter 7: Capacitors and Inductors
 - Chapter 8: Basic RL and RC circuits
 - Chapter 9: The RLC circuits
 - Chapter10: Sinusoidal steady-state analysis
 - Chapter11: AC circuit power analysis
 - Chapter12: Polyphase circuits

Chapter 1

Introduction

Four main categories of circuit analysis

- (a) DC Analysis
- (b) Transient Analysis
- (c) Sinusoidal Analysis
- (d) Frequency Analysis

Linear circuit analysis ?

TABLE 1.1 Comparison of a Linear Model for e^x to Exact Value

x	$f(x)^*$	$1 + x$	Relative error**
0.0001	1.0001	1.0001	0.0000005%
0.001	1.0010	1.001	0.00005%
0.01	1.0101	1.01	0.005%
0.1	1.1052	1.1	0.5%
1.0	2.7183	2.0	26%

*Quoted to four significant figures.

**Relative error $\triangleq \left| 100 \times \frac{e^x - (1+x)}{e^x} \right|$

Chapter 2

Basic Components and Electric Circuits

2.1 Units and Scales

2.2 Charge, Current, Voltage, and Power

2.3 Voltage and Current Sources

2.4 Ohm's Law

- Basic electrical quantities and associated units.
- Current direction and Voltage polarity
- The passive sign convention for calculation power
- Ideal voltage and current sources
- Dependent sources
- Resistance and Ohm's law

International System of Units

TABLE 2.1 SI Base Units

Base Quantity	Name	Symbol
length	meter	m
mass	kilogram	kg
time	second	s
electric current	ampere	A
thermodynamic temperature	kelvin	K
amount of substance	mole	mol
luminous intensity	candela	cd

(a) Work or Energy : Joule (J), kWh

(b) Power : Watt (W)

(c) Calorie is another unit of energy


SI Prefixes

TABLE 2.2 SI Prefixes

Factor	Name	Symbol	Factor	Name	Symbol
10^{-24}	yocto	y	10^{24}	yotta	Y
10^{-21}	zepto	z	10^{21}	zetta	Z
10^{-18}	atto	a	10^{18}	exa	E
10^{-15}	femto	f	10^{15}	peta	P
10^{-12}	pico	p	10^{12}	tera	T
10^{-9}	nano	n	10^9	giga	G
10^{-6}	micro	μ	10^6	mega	M
10^{-3}	milli	m	10^3	kilo	k
10^{-2}	centi	c	10^2	hecto	h
10^{-1}	deci	d	10^1	deka	da

Charge

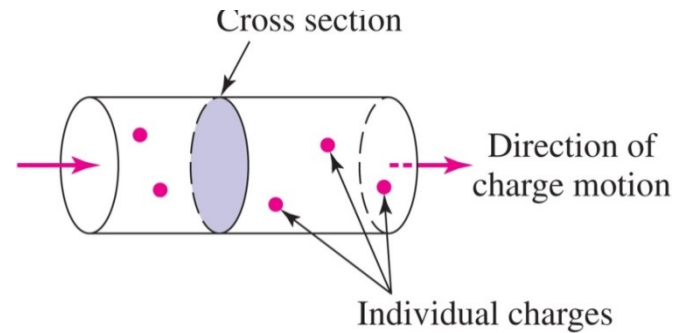- Positive or negative charge
- Unit of charge ?
- Charge of an electron ?
- Charge in motion : Current




Current

- Transfer of charge : transfer of Energy
- Controlled transfer of charge : Key factor of Electrical Engineering
- Vector quantity : amount and direction
- Reference direction of current
- Definition of 1 A :

$$i(t) = \frac{dq}{dt}$$

$$\int_{q(t_0)}^{q(t)} dq = \int_{t_0}^t i dt'$$



$$q(t) = \int_{t_0}^t i dt' + q(t_0)$$

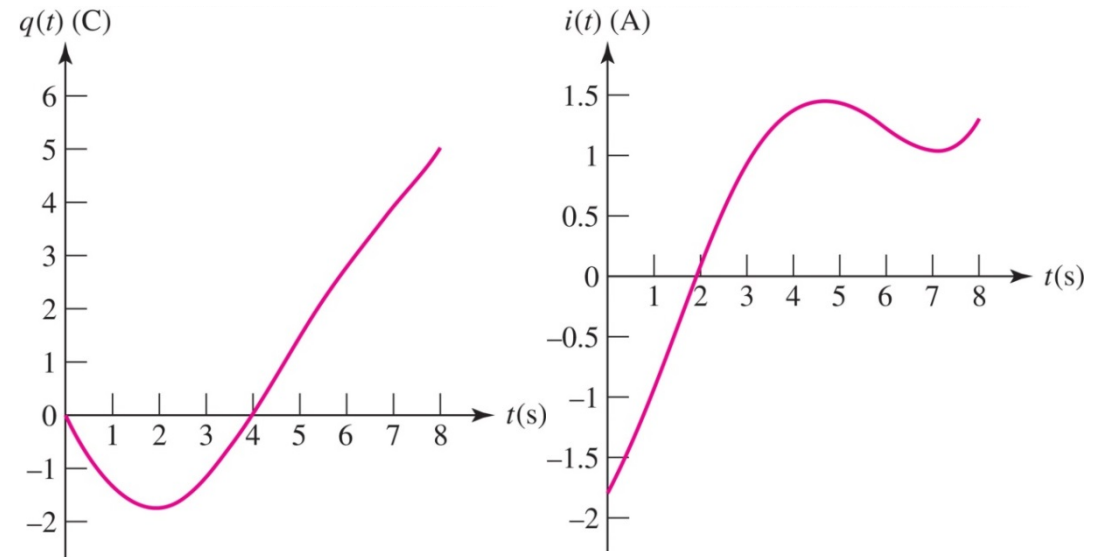

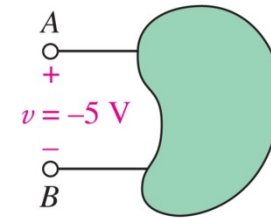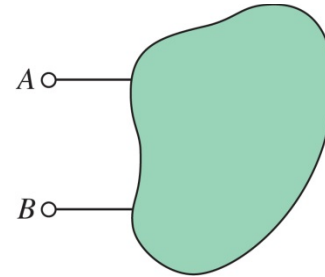
2.2 Charge, current, voltage, and power

Voltage

- Potential difference bet. two terminal :
- Can move charges
- Expenditure of Energy
- Unit of Voltage ? Volt and J/C
- Polarity convention



(a)

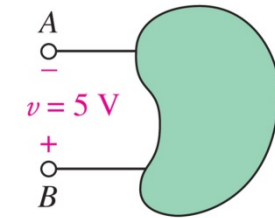



(b)

Power


- 1 Watt (J/s) : one joule of energy expenditure through transfer of one coulomb of charge in one second.
- Passive sign convention :

$$p = \upsilon i$$

The power absorbed by the element

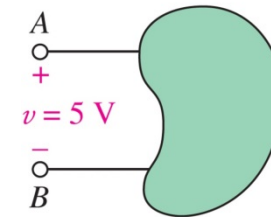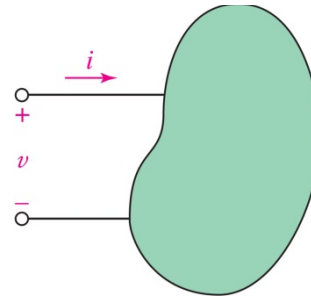


(c)

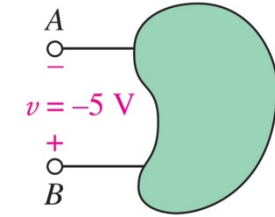


(d)

Example 2.1


The power absorbed by each element ?

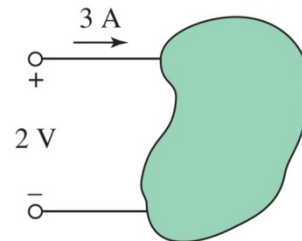

(a)

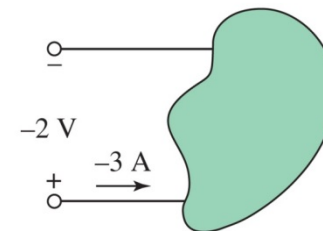

(b)

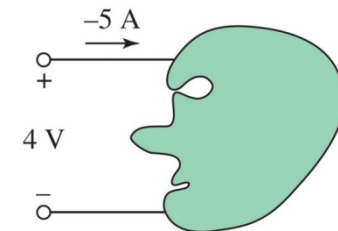


(c)

2.3 Voltage and current sources

- Simple **Lumped circuit** element model :
- Circuit element can be classified according to the relationship of the current through the element to the voltage across the element
- Voltage is proportional to the current : **Resistor**
- Voltage is proportional to the **derivative** of the current with respect to time : **Inductor**
- Voltage is proportional to the **integral** of the current with respect to time : **Capacitor**
- Voltage/current source is completely independent of the current/voltage through/through it :
Independent voltage/current sources
- Voltage or current sources that depends upon a current or voltage elsewhere in the circuit :
Dependent sources


Independent voltage sources

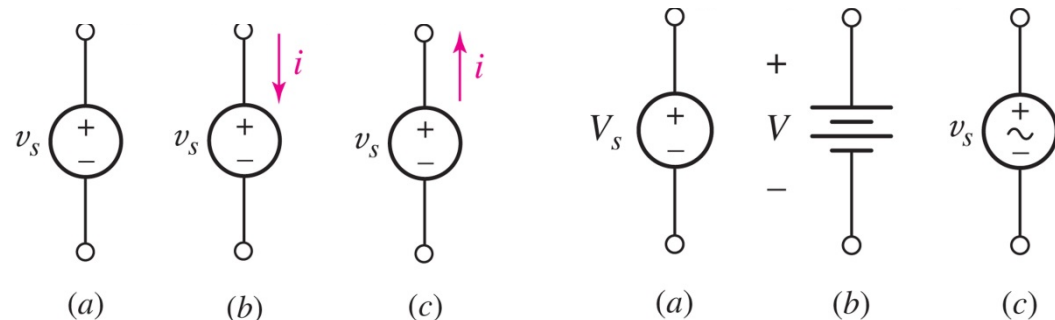- A terminal voltage which is completely independent of the current through it
- **Ideal** sources are assumed




Independent current sources

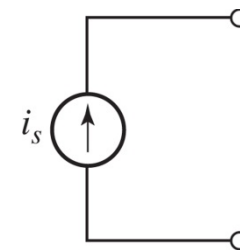- A terminal current which is completely independent of the voltage across it
- What voltage across an independent current source ?




Dependent (controlled) sources

- Useful for modeling some electronic elements
- (a) current-controlled current source
- (b) voltage-controlled current source
- (c) voltage-controlled voltage source
- (d) current-controlled voltage source
- Unit of K, g, and r ?

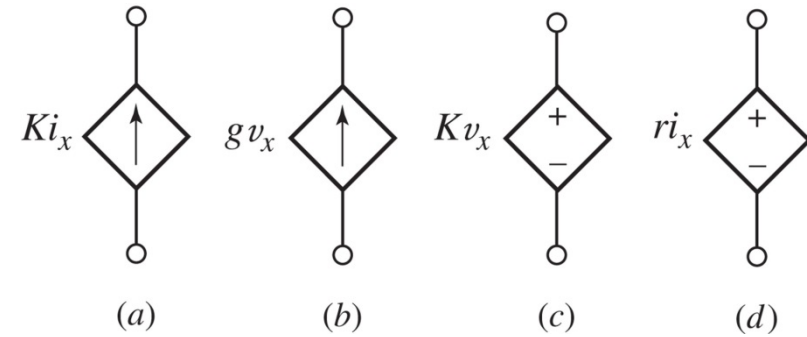


Example 2.2

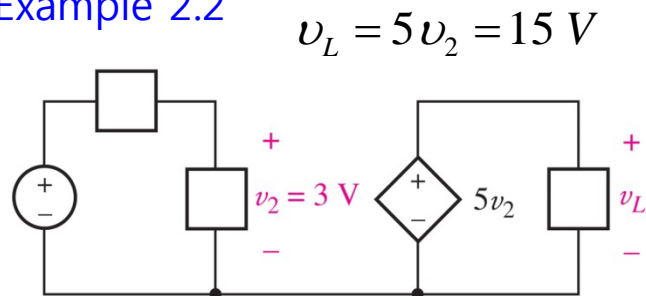


Practice 2.9

Find the power absorbed by each element.

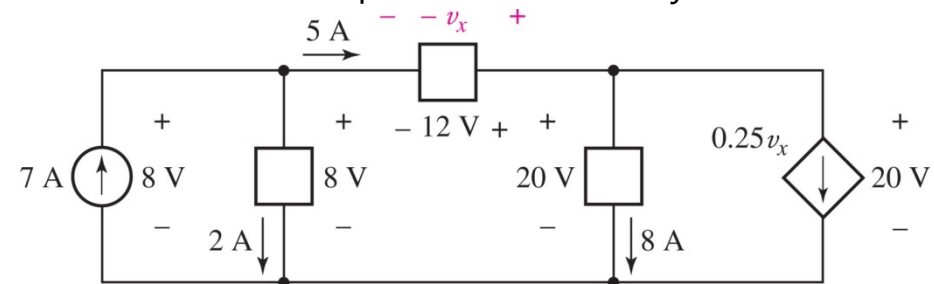

Networks and Circuits

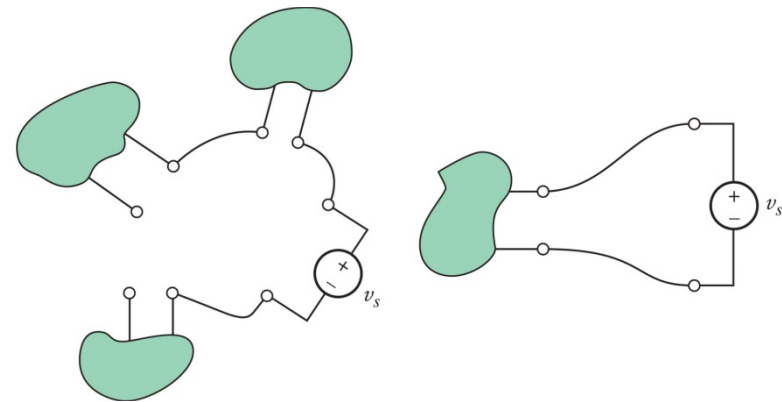- (electrical) Network : interconnection of two or more circuit elements
- (electric) Circuit : A network with at least one closed path





Resistance

- Idealized passive elements: resistor, inductor, capacitor
- Ohm's law : voltage across conducting material is directly proportional to the current through the material

$$v = Ri$$

- Proportionality factor R : Resistance
- Unit of resistance : ohm (Ω) = V/A
- Linear resistor : constant within certain range of current and voltage or power
- Nonlinear resistor : active element such as diode, transistor
- The absorbed power :

$$p = vi = i^2R = v^2 / R$$

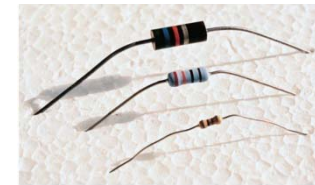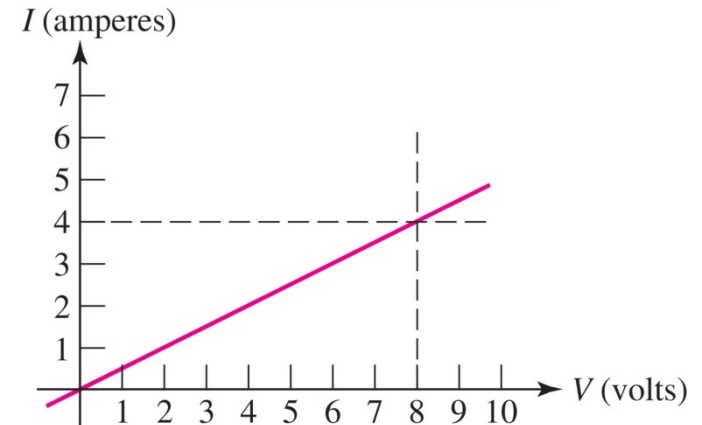


(a)




(b)

Resistivity

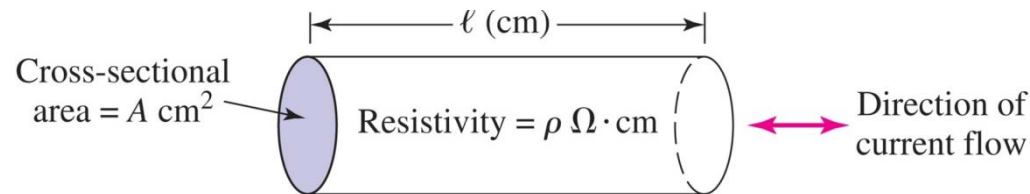

$$R = \rho \frac{l}{A}$$

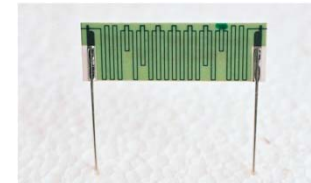- Resistivity is an inherent property of a material



Conductance

- Reciprocal of Resistance

$$G = \frac{i}{v} = \frac{1}{R}$$

- Unit of conductance : siemens (S) = mho = A/V
- Instantaneous voltage, current, and power
- Short or open circuit for zero or infinite resistance

Homework : 2장 Exercises 4의 배수 문제 (48번까지만)

- Due day : 2장 수업 끝나고 일주일 후 수업시작 전까지 제출.

이 자료에 나오는 모든 그림은 McGraw-hill 출판사로부터 제공받은 그림을 사용하였음.

All figures at this slide file are provided from The McGraw-hill company.