

Yongsug Suh



Power Electronics - Lecture 3




**CHONBUK
NATIONAL UNIVERSITY**

Lecture 3 – Three-phase Systems

- Contents
 - Phasor representation in three-phase system
 - Power definitions in three-phase system
 - Advantages of three-phase system


Three-Phase System – Wye connection

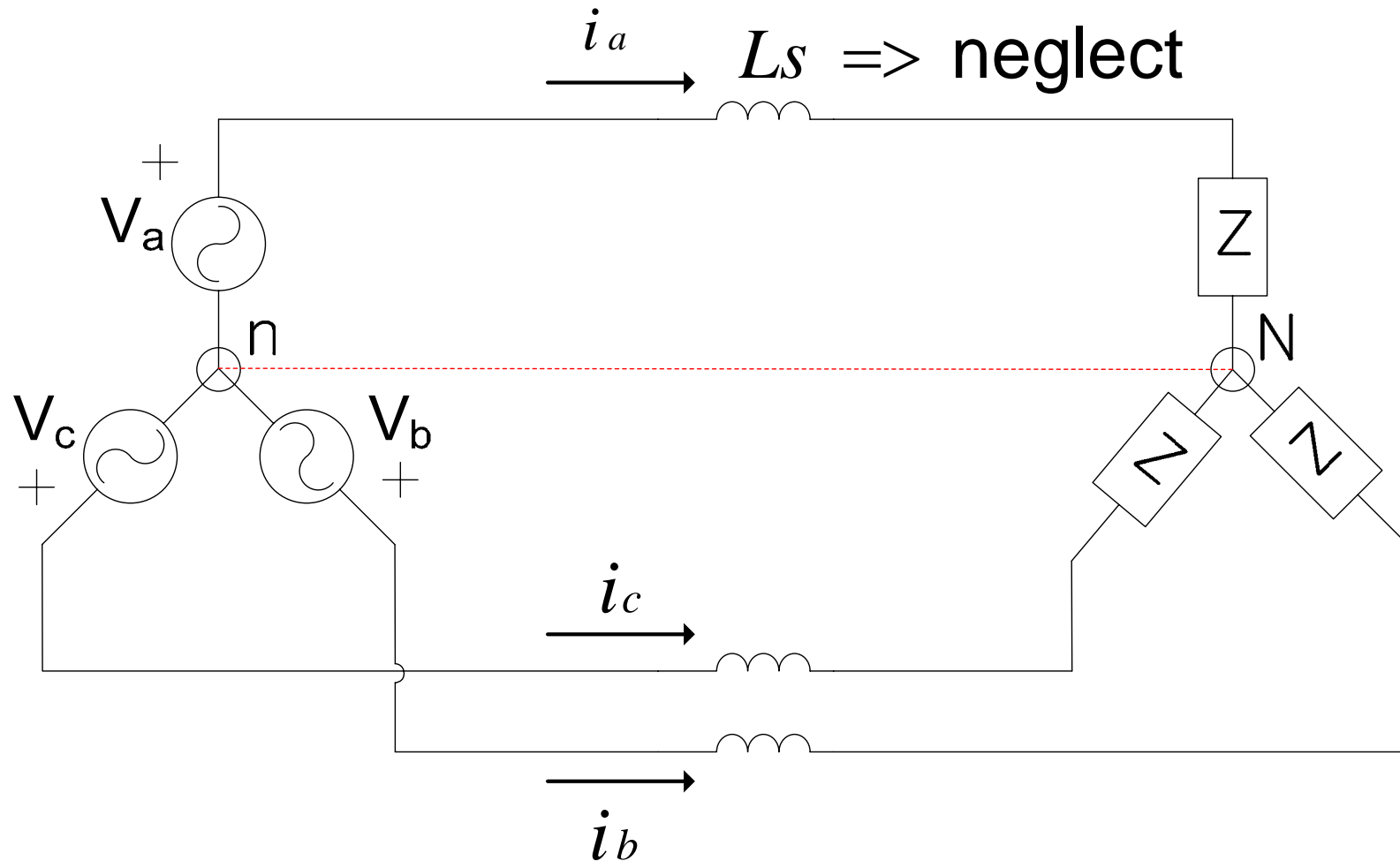

✱ $V_{nN}=0$ under balanced system

Three-Phase System

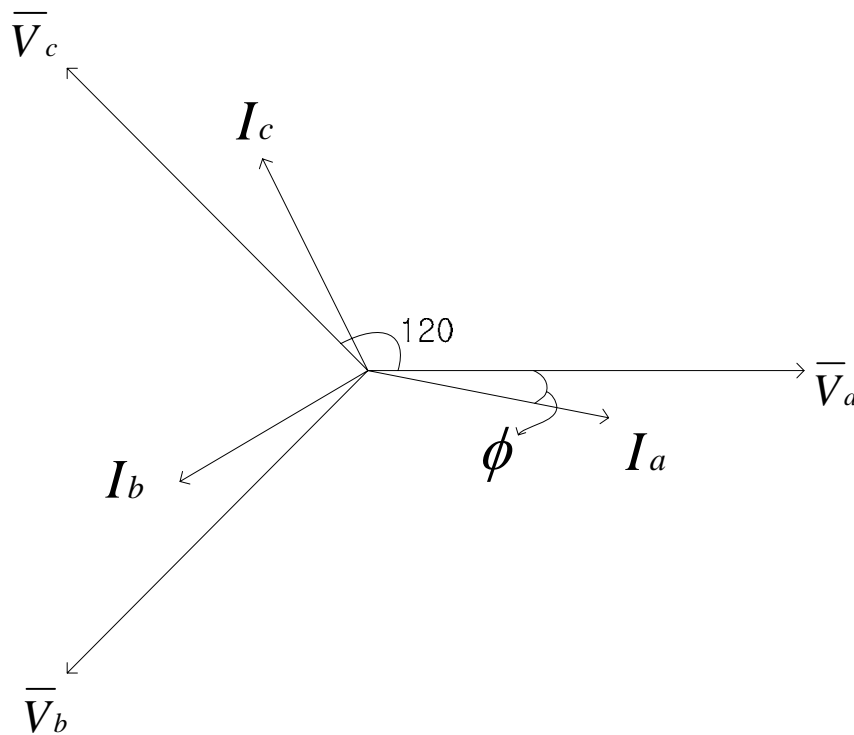– Phasor representation of balanced system



$$v_a = \sqrt{2}V \cos \omega t$$

$$v_b = \sqrt{2}V \cos(\omega t - 120^\circ)$$

$$v_c = \sqrt{2}V \cos(\omega t + 120^\circ)$$

$$i_a = \sqrt{2}I \cos(\omega t - \phi)$$

$$i_b = \sqrt{2}I \cos(\omega t - \phi - 120^\circ)$$

$$i_c = \sqrt{2}I \cos(\omega t - \phi + 120^\circ)$$

■ Phasor representation

$$\mathbf{V}_a = V e^{j0}, \quad \mathbf{V}_b = V e^{j(-120^\circ)}, \quad \mathbf{V}_c = V e^{j(120^\circ)}$$

$$\mathbf{I}_a = I e^{-j\phi}, \quad \mathbf{I}_b = I e^{-j(\phi+120^\circ)}, \quad \mathbf{I}_c = I e^{-j(\phi-120^\circ)}$$

Power Definitions for Three-phase System

- Instantaneous active power $\overset{\Delta}{=} p(t) = v_a i_a + v_b i_b + v_c i_c$
- Instantaneous reactive power $\overset{\Delta}{=} q(t) = v_a' i_a + v_b' i_b + v_c' i_c$
- Complex power $\overset{\Delta}{=} \mathbf{S} = \mathbf{V}_a \mathbf{I}_a^* + \mathbf{V}_b \mathbf{I}_b^* + \mathbf{V}_c \mathbf{I}_c^*$
- Apparent power $\overset{\Delta}{=} |\mathbf{S}| = 3VI$
- Average of instantaneous active power, P_{av}

90° phase delayed of v_a
 $= \sqrt{2}V \cos(\omega t - 90^\circ)$

$$\overset{\Delta}{=} \frac{1}{T} \int_T p(t) dt = \text{Re}[\mathbf{S}] = 3VI \cos \phi$$

- Average of instantaneous reactive power, Q_{av}

$$\overset{\Delta}{=} \frac{1}{T} \int_T q(t) dt = \text{Im}[\mathbf{S}] = 3VI \sin \phi$$

Advantages of Three-phase System

- $S = P_{av} + jQ_{av}$
 $p(t) = P_{av}$ } “Instantaneous active power, $p(t)$ is constant having the same value as the average real power(P_{av}) under balanced system”

- Advantages of three-phase system

- $p(t) = P_{av}$; no ripple component under balanced condition

- **Number of wires = 3 ;**
1 - ϕ - > 2 wires
2 - ϕ - > 3 wires

- Three-phase system may require additional wire to carry small-sized common-mode neutral current

MISSION

The Laboratory performs the research and educational activity in the area of electrical system that can be applied in environmental-friendly & sustainable energy conversion process.

